

Digital Integrated Circuits

#Homework 1 2024.09.20 (Due: 09.27 15:30 ED520)



Given $V_{DD}=0.9V$, $W_{min}=64nm$, $L_{min}=32nm$ with resolution of 1nm; there are three kinds of V_t : High V_t , Medium V_t and Low V_t CMOS

(1) MOS and Inverter with medium threshold voltages (30%)

- Run SPICE to draw the I-V DC curves for PMOS and NMOS with minimum feature size using High V_t , Medium V_t , and Low V_t respectively. (24%)
- Keep L equals to L_{min} , design the W of each transistor using medium V_t such that the logic threshold of inverter is at $0.5V_{DD}$. **Discuss your design procedures** and the way you choose your MOS dimensions. Run SPICE to verify your results. (6%)

  (2) Design a CMOS schmitt trigger shown at Fig. 1(b) such that $V^+ = 0.54-0.57V$ and $V^- = 0.36-0.33V$ with $CT=V_{DD}$ (70%)

- Discuss the difference between Fig. 1(a) and (b).** Give the W/L of each device (in table form) of Fig. 1(b) with $CT=V_{DD}$ and **discuss your design procedures** to determine the size of each transistor using medium V_t . (30%)
- Run SPICE to verify your results. Your report must have the figures of VTC, I_{N2} vs V_{in} , and I_{N4} vs V_{in} (20%)
- Use the same size as in part A, and modify CT to $0.8V_{DD}$. Repeat part B to have figures to indicate the new V^- and V^+ (20%)



(b) Schmitt trigger with controllable hysteresis

Fig. 1 Schmitt Trigger Circuit