Digital Integrated Circuits

Hspice Example

Advisor: Prof. Yi-Chung Wu (yicwu@nycu.edu.tw)

Credited by: Shyh-Jye Jerry Jou


Institute of Electronics, National Yang Ming Chiao Tung University





Basic(1/2)

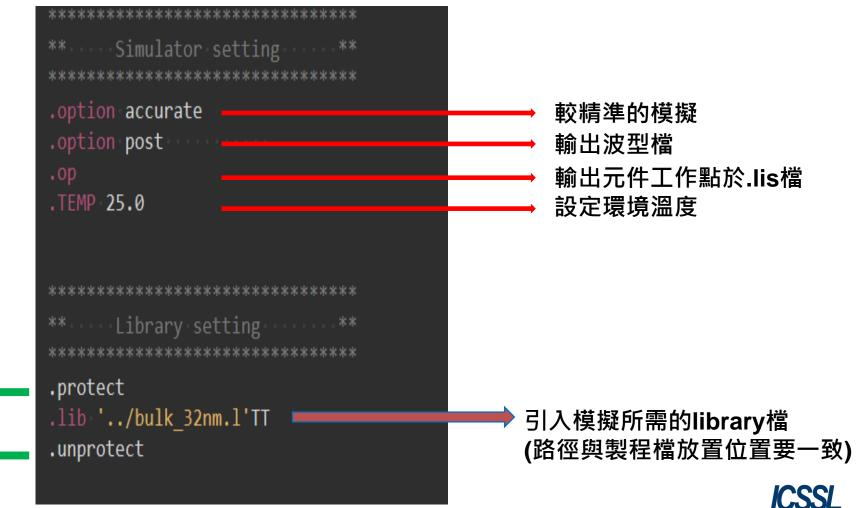Hspice範例code請至以下路徑複製:
 /RAID2/COURSE/dic/dicTA01/dic_2024_spring/Tutorial_Example



包含在裡頭的檔案資訊 不會秀在.lis檔

Basic(2/2)

```
param xvdd = 0.9
param xvss = 0
param wp = 64n
 param wn = 64n
param cycle = 1n
 param simtime = 5n
subckt inv in out vdd vss
m1 out in vdd vdd pmos w=wp l=32n
m2 out in vss vss nmos w=wn l=32n
                                   (呼叫mos的方式: m?? D G S B pmos/nmos w=? l=?)
xinv_1 input output vdd vss inv
                                  → 建立主電路(呼叫子電路用x開頭;呼叫電容用c開頭)
cload output vss 5f
     Power declaration
vvdd
                     xvdd
                                 DC電壓源
                     xvss
        VSS
VVSS
                                                                    呼叫電壓源用v開頭
                                                                   pulse電壓源
                0 pulse(xvdd 0 1n 0.1n 0.1n 'cycle*0.45' cycle)=
        input
vin-
```


DC Analysis

```
.option accurate
.option post
.TEMP 25.0
.protect
.lib '../bulk 32nm.l'TT
.unprotect
.param xvdd = 0.9
.param xvss = 0
.param wp = 64n
.param wn = 64n
.param cycle = 1n
.param simtime = 5n
.subckt inv in out vdd vss
m1 out in vdd vdd pmos w=wp l=32n
m2 out in vss vss nmos w=wn l=32n
xinv 1 input output vdd vss inv
cload output vss 5f
```

對vin電壓源從0v到0.9v以step=0.01v做DC分析 (sweep wp變數,從wp=100n開始,每step=100n 重複模擬一次到wp=1000n)



尋找輸出: .sw0檔案 (for DC analysis)

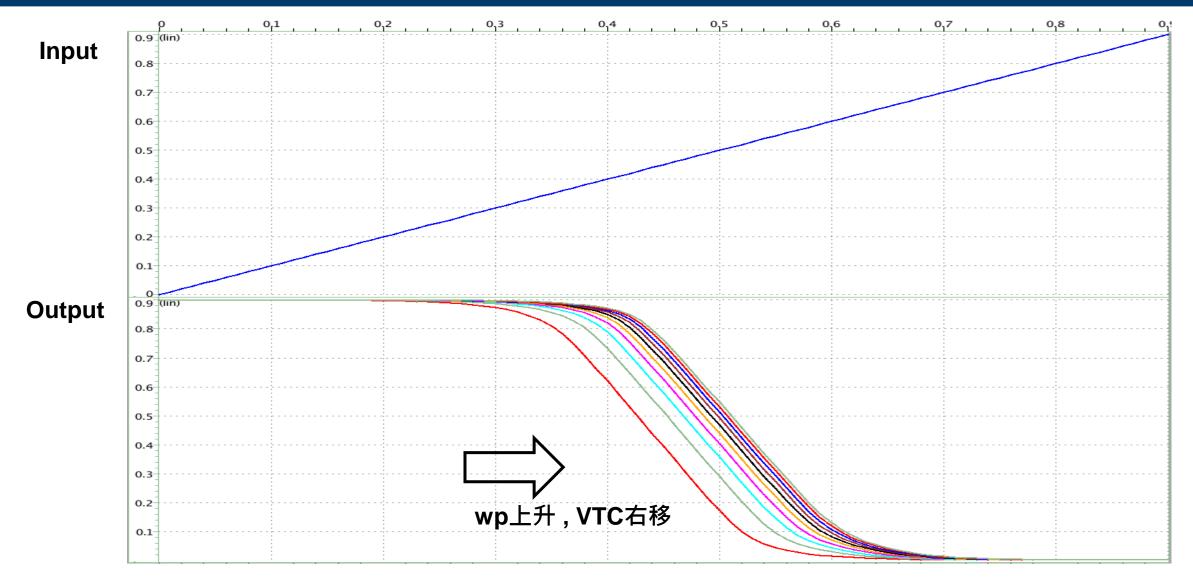


Transient Analysis

```
.option accurate
 .option post
 .TEMP 25.0
 .protect
.lib '../bulk 32nm.l'TT
 .unprotect
 .param xvdd = 0.9
 .param xvss = 0
param wp = 64n
 .param wn = 64n
 .param cycle = 1n
 .param simtime = 5n
 .subckt inv in out vdd vss
m1 out in vdd vdd pmos w=wp l=32n
m2 out in vss vss nmos w=wn l=32n
xinv 1 input output vdd vss inv
cload output vss 5f
```

以1ps的間隔模擬總共simtime的時間做暫態分析 (sweep wp變數,從wp=64n開始每step=64n重 複做一次模擬到wp=384n)



尋找輸出: .tr0檔案 (for Transient analysis)

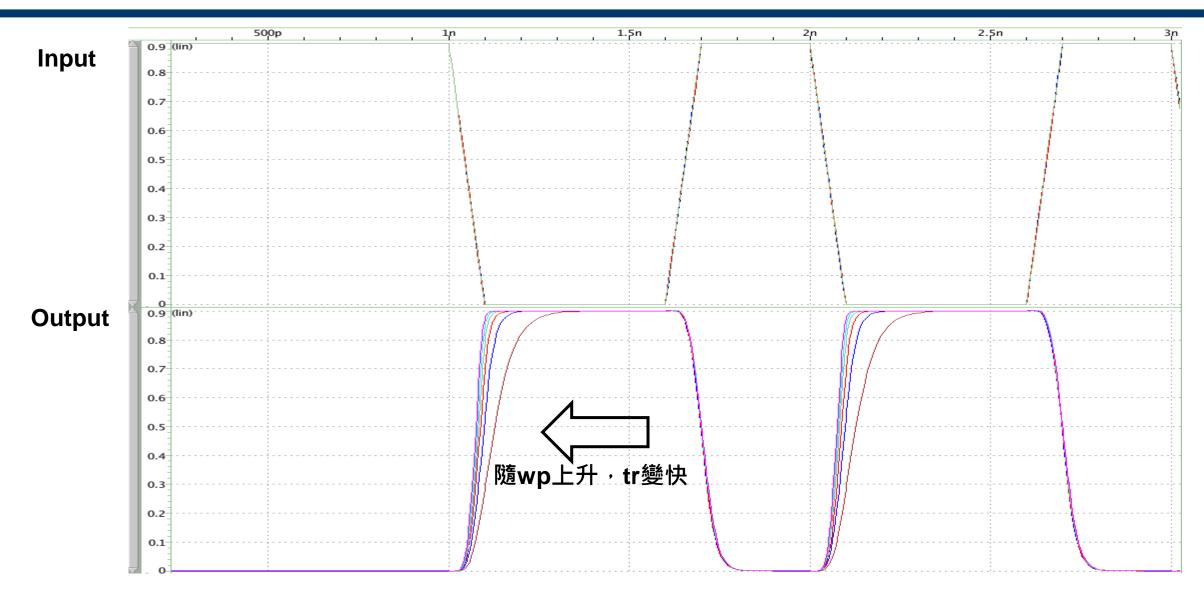

執行模擬指令以及開啟波形軟體

```
ee05 [dicta01/example_1]%
                                                                   ee05 [dicta01/example_1]%
ee05 [dicta01/example 1]%
                                                                   ee05 [dicta01/example 1]%
ee05 [dicta01/example 1]%
                                                                   ee05 [dicta01/example 1]%
ee05 [dicta01/example 1]%
                                                                   ee05 [dicta01/example 1]%
ee05 [dicta01/example_1]%
                                                                   ee05 [dicta01/example 1]%
ee05 [dicta01/example 1]%
                                                            or
                                                                   ee05 [dicta01/example 1]%
ee05 [dicta01/example_1]%
                                                                   ee05 [dicta01/example_1]%
ee05 [dicta01/example 1]% hspice -i example dc.sp
                                                                        [dicta01/example_1]% hspice -i example_dc.sp -o
                                                                          不會輸出.lis檔案(但會顯示在螢幕上)
   example dc.ic0
   example dc.sw0
   example_dc.pa0
                                                                   linux15 [dicta02/example]%
   example dc.st0
                                                                   linux15 [dicta02/example]%
   example tran.tr0
                                                                   linux15 [dicta02/example]%
   example_tran.ic0@0
                                                                   linux15 [dicta02/example]% wv &
   example_tran.ic0
   example tran.pa0
   example_tran.st0
                                                                            開啟波形軟體
   example_tran.sp
   example_dc.sp
```